


Maserati 6 Cyl. Hook-up of Ignition Coils

By Walter Loeliger

FALL 1990

After I had some work done on my Mistral ignition, the car wouldn't run. When I checked the wiring diagram with others, I discovered that the Mistral wiring diagram was wrong. I have corrected it as shown.

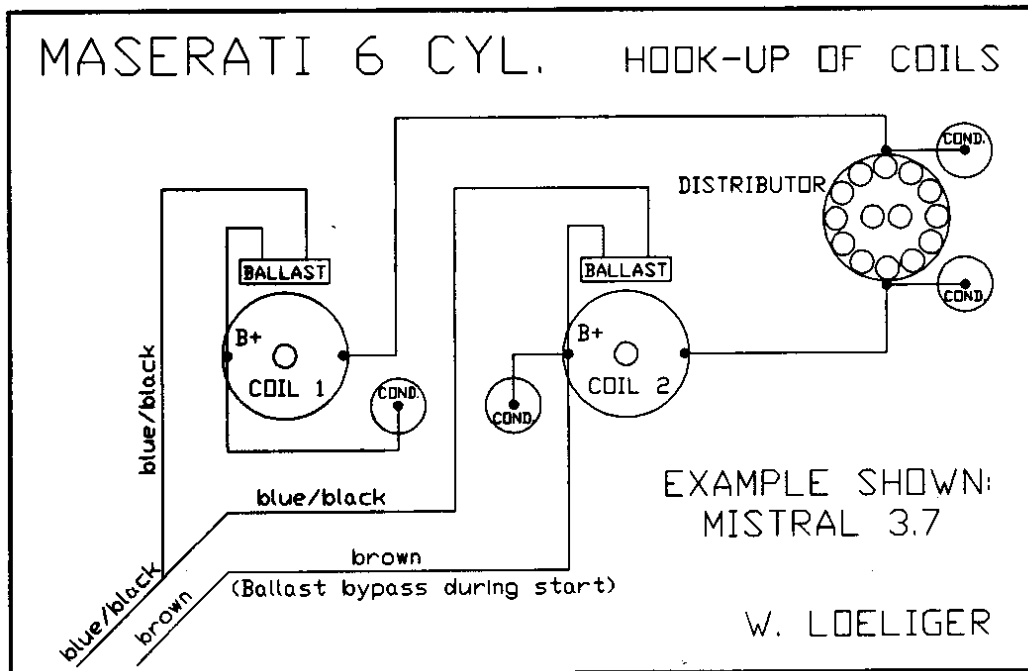Make a copy of the enlarged detail of the revised Mistral wiring diagram on the facing page and attach it to yours. The detail below shows the actual location of the components in the engine compartment, and how they should be correctly hooked up.



109/A

Mistral: Detail of Wiring Diagram Ign. Coils
revised 5-2-90 Lee

